
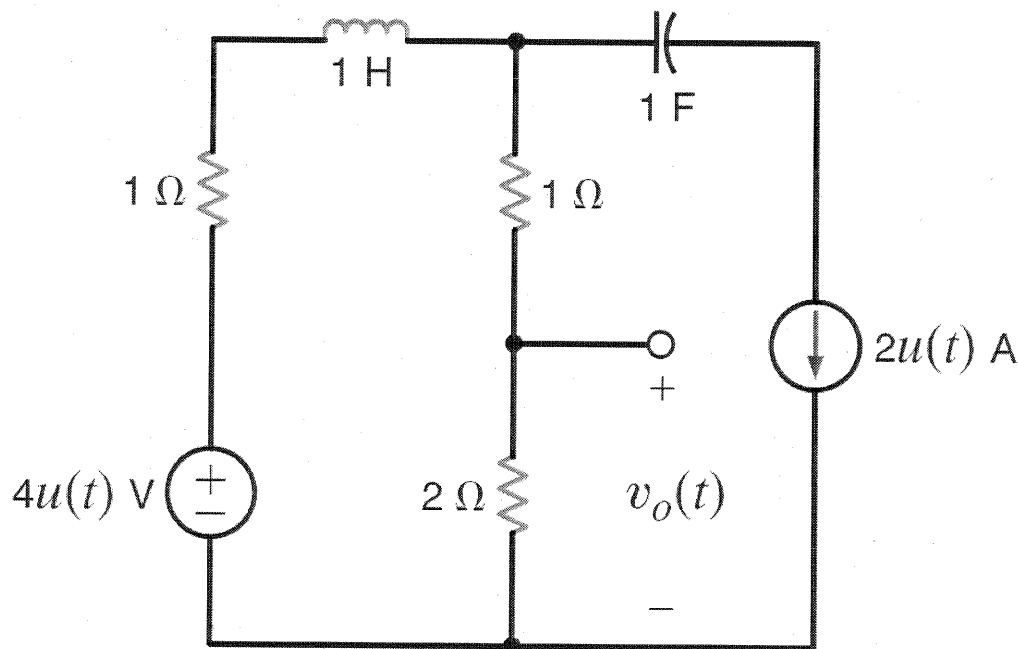


**14.10** Use nodal analysis to find  $v_o(t)$ ,  $t > 0$ , in the network in Fig. P14.10. **PSV**

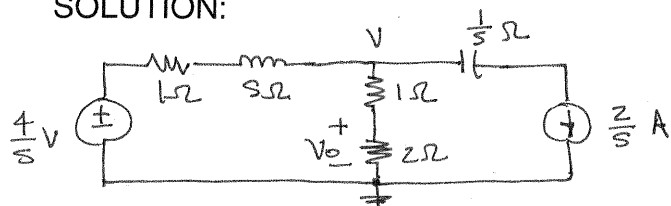

**Figure P14.10**

**SOLUTION:**



$$\frac{V - 4/s}{s+1} + \frac{V}{3} + \frac{2}{s} = 0$$

$$V \left[ \frac{1}{s+1} + \frac{1}{3} \right] = \frac{4}{s(s+1)} - \frac{2}{s}$$

$$V \left[ \frac{3 + s + 1}{3(s+1)} \right] = \frac{-2s + 2}{s(s+1)} \Rightarrow V(s) = \frac{6(-s+1)}{s(s+4)} \quad v_o = \frac{2}{3} V$$

$$V_o(s) = \frac{4(-s+1)}{s(s+4)} = \frac{1}{s} - \frac{5}{s+4}$$

$$v_o(t) = [1 - 5e^{-4t}]u(t)$$