

14.21 Use Thévenin's theorem to find $v_o(t)$, $t > 0$, in the network in Fig. P14.21. **CS**


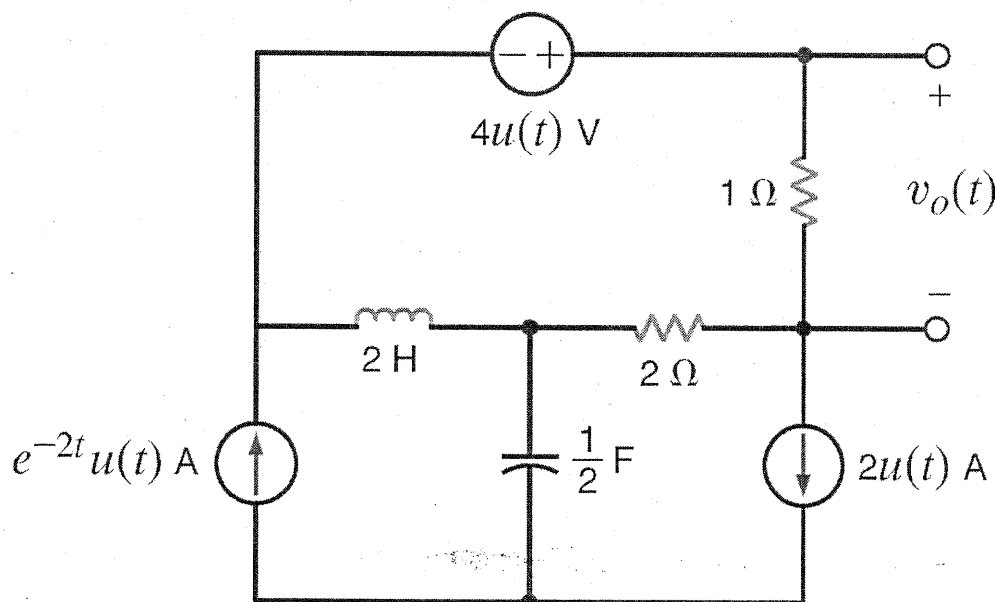


Figure P14.21

SOLUTION:

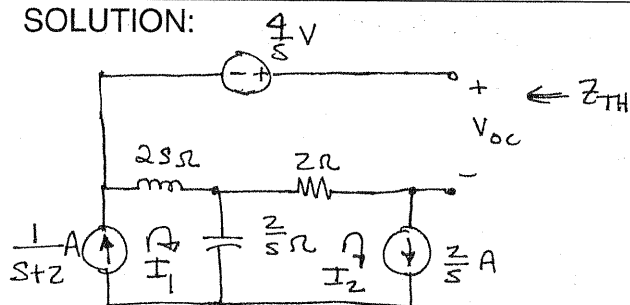


$$I_1 = \frac{1}{s+2} \quad I_2 = \frac{2}{s}$$

$$\frac{4}{s} = V_{oc} - 2I_2 - 2sI_1$$

$$V_{oc} = \frac{4}{s} + \frac{4}{s} + \frac{2s}{s+2} = \frac{8}{s} + \frac{2s}{s+2}$$

$$V_{oc} = \frac{2s^2 + 8s + 16}{s(s+2)}$$

$$Z_{TH} = 2s + 2$$

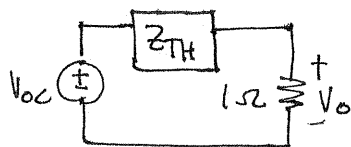

$$V_o = \frac{V_{oc}(1)}{1 + Z_{TH}} = \frac{2(s^2 + 4s + 8)}{s(s+2)(s+1.5)} = \frac{s^2 + 4s + 8}{s(s+1.5)(s+2)} = \frac{8/3}{s} - \frac{17/3}{s+1.5} + \frac{4}{s+2}$$

$$v_o(t) = \left[\frac{8}{3} - \frac{17}{3}e^{-1.5t} + 4e^{-2t} \right] u(t) \text{ V}$$