

**14.23** Use Thévenin's theorem to determine  $i_o(t)$ ,  $t > 0$ , in the circuit shown in Fig. P14.23. **PSV**


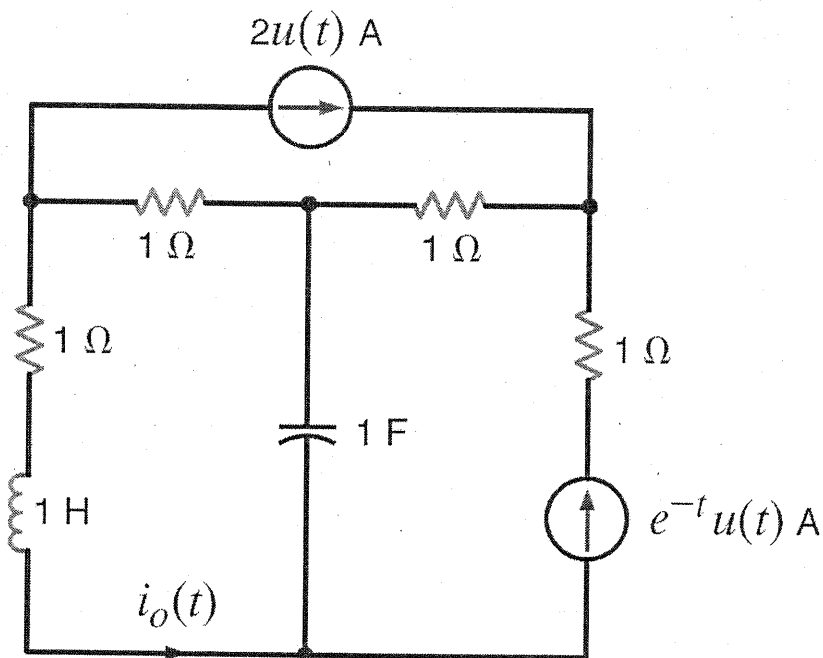
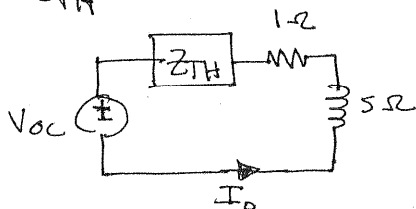


Figure P14.23

SOLUTION:

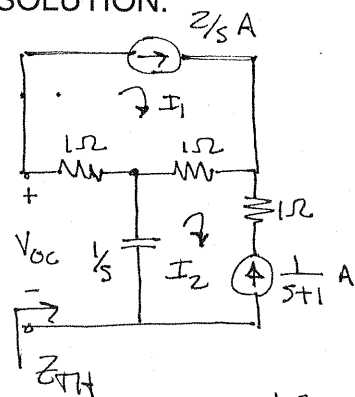

$$I_1 = \frac{2}{s} \quad I_2 = -\frac{1}{s+1}$$

$$V_{OC} = (1)(-I_1) - \frac{1}{s} I_2 = -\frac{2}{s} + \frac{1}{s(s+1)} = \frac{-(2s+1)}{s(s+1)}$$

$$Z = 1 + 1/s = (s+1)/s$$

$$I_o = \frac{-V_{OC}}{Z + 1/s} = \frac{-(2s+1)}{(s+1)^3}$$

$$I_o = \frac{k_1}{(s+1)^3} + \frac{k_2}{(s+1)^2} + \frac{k_3}{s+1} = \frac{-1}{(s+1)^3} + \frac{2}{(s+1)^2}$$

$$i_o(t) = \left[ 2te^{-t} - \frac{1}{2}t^2e^{-t} \right] u(t) \text{ A}$$