
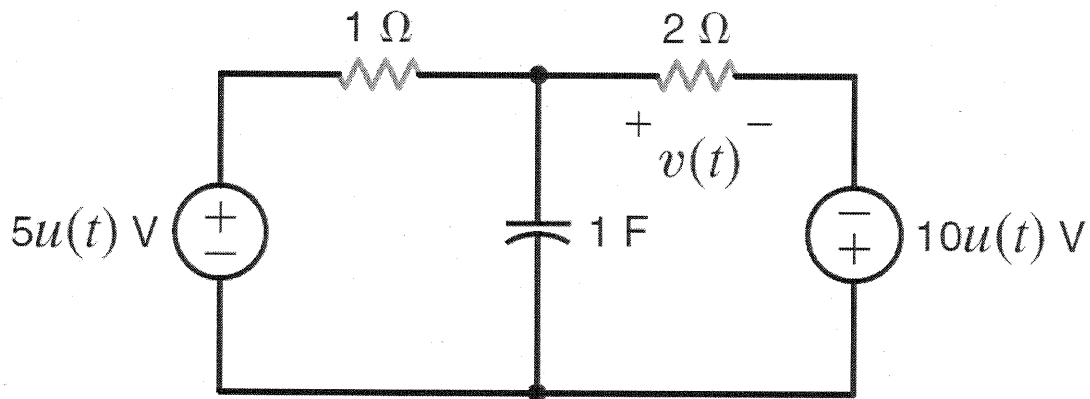


**14.4** Use Laplace transforms to find  $v(t)$  for  $t > 0$  in the network shown in Fig. P14.4. Assume zero initial conditions.

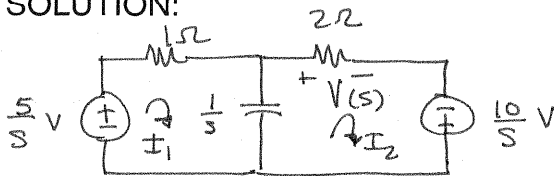

**Figure P14.4**

**SOLUTION:**



$$\frac{5}{s} = I_1(s) \left[ 1 + \frac{1}{s} \right] - I_2(s) \left( \frac{1}{s} \right)$$

$$\frac{10}{s} = -I_1(s) \left( \frac{1}{s} \right) + I_2(s) \left[ 2 + \frac{1}{s} \right]$$

$$\text{or, } \begin{cases} 5 = I_1(s+1) - I_2 \\ 10 = -I_1 + I_2(2s+1) \end{cases} \quad \left. \begin{array}{l} I_1 = 5/s \\ I_2 = 5/s \end{array} \right\}$$

$$V(s) = 2 I_2(s) = \frac{10}{s}$$

$$\boxed{v(t) = 10 u(t)}$$