

14.7 For the network shown in Fig. P14.7, find $i_o(t)$, $t > 0$.

CS


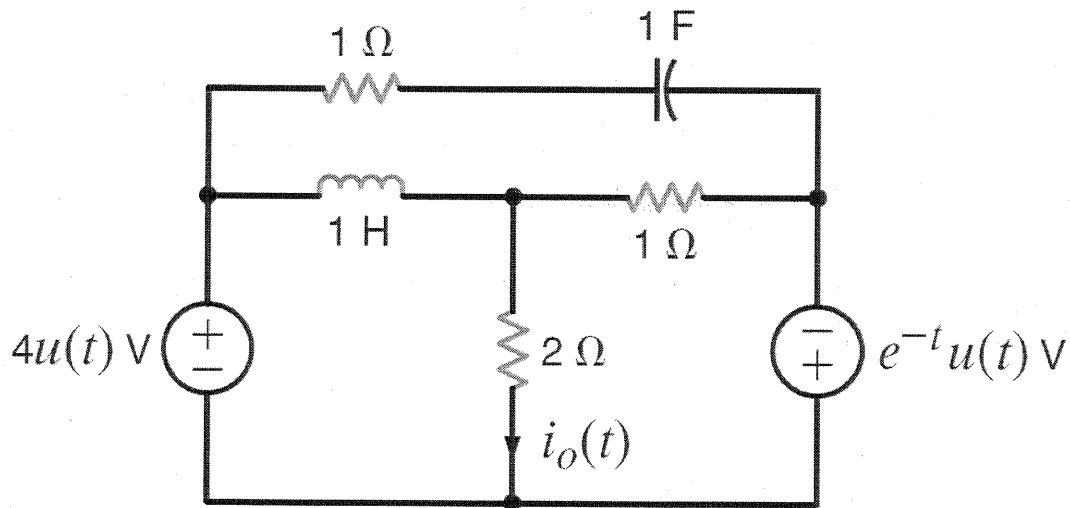


Figure P14.7

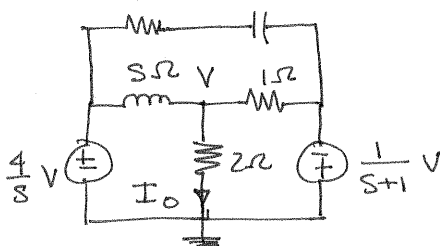SOLUTION: $t=0^-$: No excitation. So, all initial conditions = 0.



$$\frac{V - 4/s}{s} + \frac{V + \frac{1}{s+1}}{1} + \frac{V}{2} = 0$$

$$V \left(\frac{1}{s} + \frac{3}{2} \right) = \frac{4}{s^2} - \frac{1}{s+1}$$

$$V = \frac{2(-s^2 + 4s + 4)}{s(s+1)(3s+2)}$$

$$I_o = V/2 = \frac{1/3(-s^2 + 4s + 4)}{s(s+1)(s+2/3)} = \frac{K_1}{s} + \frac{K_2}{s+1} + \frac{K_3}{s+2/3}$$

$$K_1 = 2 \quad K_2 = -1 \quad K_3 = -4/3$$

$$i_o(t) = \left[2 - e^{-t} - \frac{4}{3}e^{-(2/3)t} \right] u(t) \quad \checkmark$$